




# Working of 555 Timer (Unit IV)

Prof Suneeta S. Raykar,  
Associate Professor E&E GEC  
Suneeta@gec.ac.in


# Configuration of 555 as a astable multivibrator

555 IC Timer Block Diagram

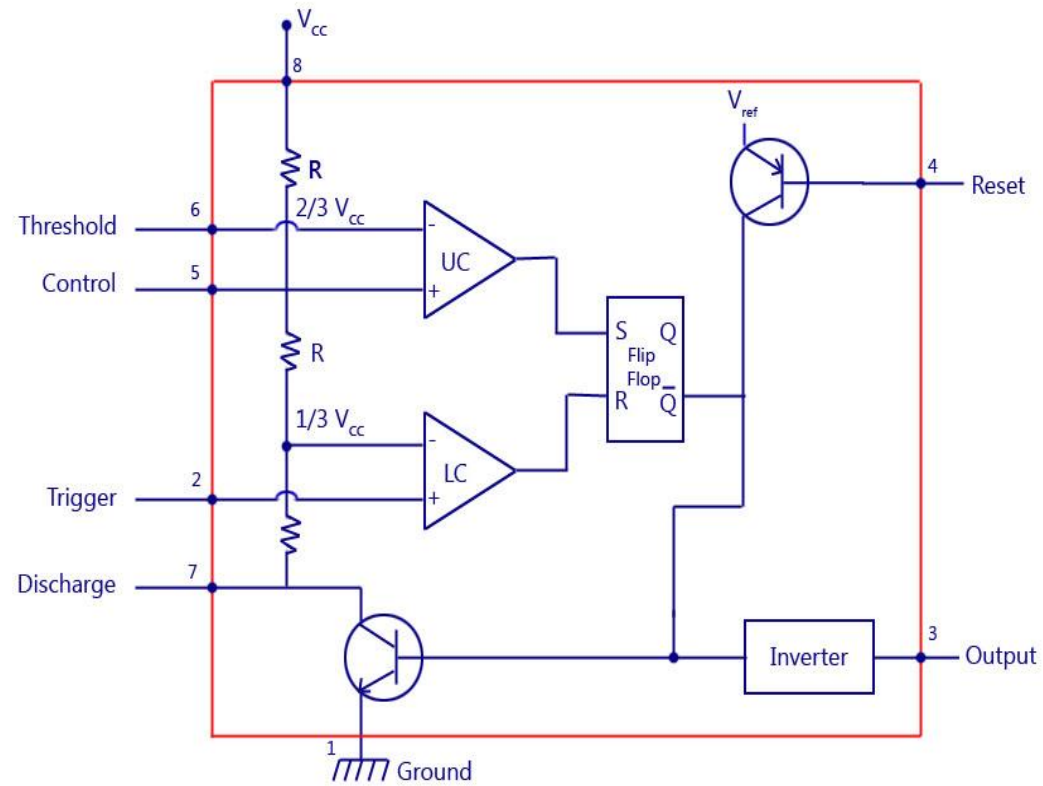


[www.CircuitsToday.com](http://www.CircuitsToday.com)

Astable Multivibrator using 555 Timer

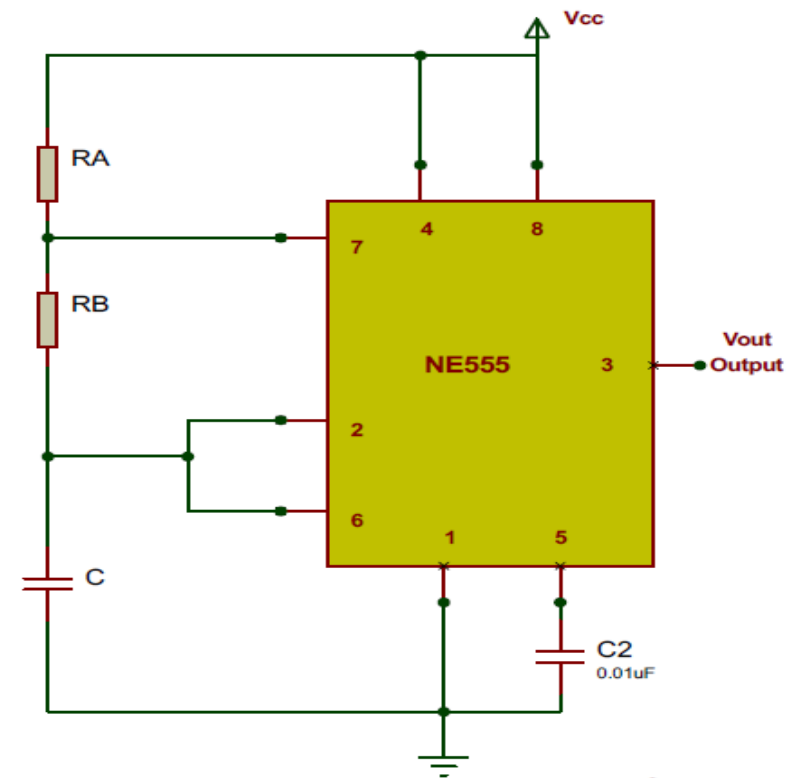


[www.CircuitsToday.com](http://www.CircuitsToday.com)

# Working of 555 as astable

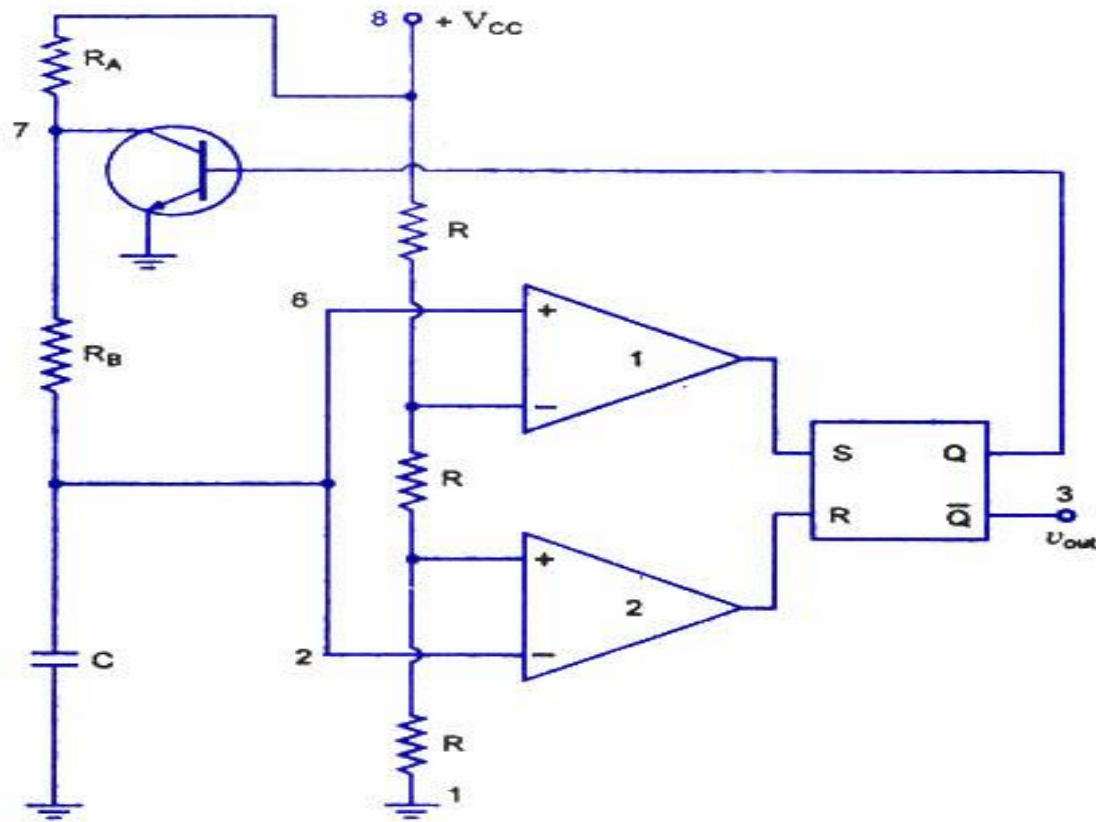

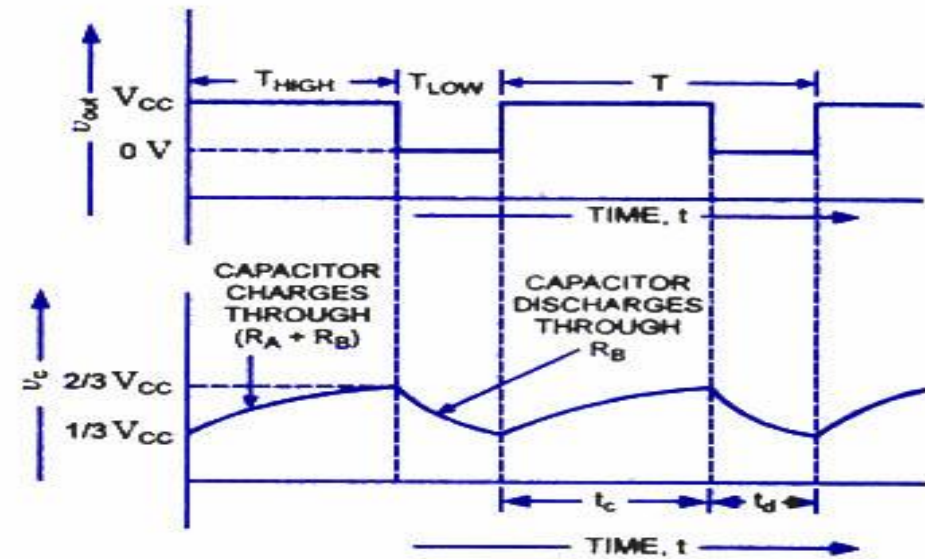*Internal Circuitry With External Connections*




*Capacitor and Output Voltage Waveforms*

*Astable Operation*

# 555 as monostable multivibrator

555 IC Timer Block Diagram

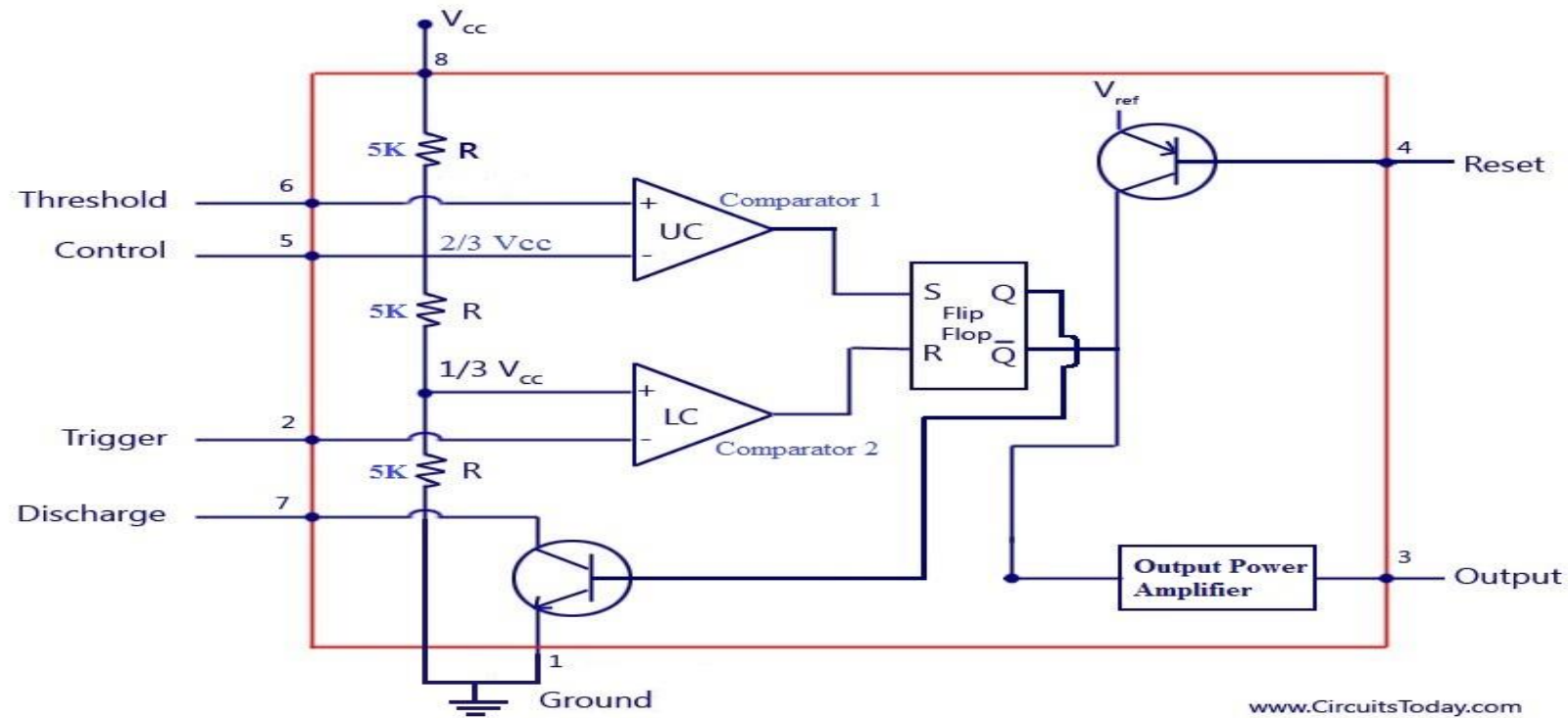

# Derivation

- The time during which the capacitor C charges from  $1/3 V_{CC}$  to  $2/3 V_{CC}$  is equal to the time the output is high and is given as  $t_c$  or  $T_{HIGH} = 0.693 (R_A + R_B) C$ , which is proved below.
- Voltage across the capacitor at any instant during charging period is given as,
- $v_c = V_{CC}(1 - e^{-t/RC})$
- The time taken by the capacitor to charge from 0 to  $+1/3 V_{CC}$

$$1/3 V_{CC} = V_{CC}(1 - e^{-t/RC})$$

The time taken by the capacitor to charge from 0 to  $+2/3 V_{CC}$

- or  $t_2 = RC \log_e 3 = 1.0986 RC$

So the time taken by the capacitor to charge from  $+1/3 V_{CC}$  to  $+2/3 V_{CC}$

- $t_c = (t_2 - t_1) = (1.0986 - 0.405) RC = 0.693 RC$

Substituting  $R = (R_A + R_B)$  in above equation we have

- $T_{HIGH} = t_c = 0.693 (R_A + R_B) C$
- where  $R_A$  and  $R_B$  are in ohms and C is in farads.

# Derivation

- The time during which the capacitor discharges from  $+2/3 V_{CC}$  to  $+1/3 V_{CC}$  is equal to
- the time the output is low and is given as
- **$t_d$  or  $T_{LOW} = 0.693 R_B C$**  where  $R_B$  is in ohms and  $C$  is in farads The above equation is worked out as follows: Voltage across the capacitor at any instant during discharging period is given as
- **$v_c = 2/3 V_{CC} e^{-t_d / R_B C}$**
- Substituting  $v_c = 1/3 V_{CC}$  and  $t = t_d$  in above equation we have
- **$+1/3 V_{CC} = +2/3 V_{CC} e^{-t_d / R_B C}$**
- Or  **$t_d = 0.693 R_B C$**

# Final equation



- Overall period of oscillations,  $T = T_{\text{HIGH}} + T_{\text{LOW}} = 0.693 (R_A + 2R_B) C$ , The frequency of oscillations being the reciprocal of the overall period of oscillations  $T$  is given as
- $f = 1/T = 1.44 / (R_A + 2R_B) C$
- Equation indicates that the frequency of oscillation  $f$  is independent of the collector supply voltage  $+V_{CC}$ .
- Often the term duty cycle is used in conjunction with the astable multivibrator.
- *The duty cycle, the ratio of the time  $t_c$  during which the output is high to the total time period  $T$  is given as*
- % duty cycle,  $D = t_c / T * 100 = (R_A + R_B) / (R_A + 2R_B) * 100$



# Square wave generator using 555 astable

- From the above equation it is obvious that square wave (50 % duty cycle) output can not be obtained unless  $R_A$  is made zero. However, there is a danger in shorting resistance  $R_A$  to zero. With  $R_A = 0$  ohm, terminal 7 is directly connected to  $+V_{CC}$ . During the discharging of capacitor through  $R_B$  and transistor, an extra current will be supplied to the transistor from  $V_{CC}$  through a short between pin 7 and  $+V_{CC}$ . It may damage the transistor and hence the timer.
- The capacitor  $C$  charges through  $R_A$  and diode  $D$  to approximately  $+2/3V_{CC}$  and discharges through resistor  $R_B$  and terminal 7 (transistor) until the capacitor voltage drops to  $1/3 V_{CC}$ .
- Then the cycle is repeated. To obtain a square wave output,  $R_A$  must be a combination of a fixed resistor  $R$  and a pot, so that the pot can be adjusted to give the exact square wave.

# Practical working (Blinking LED)

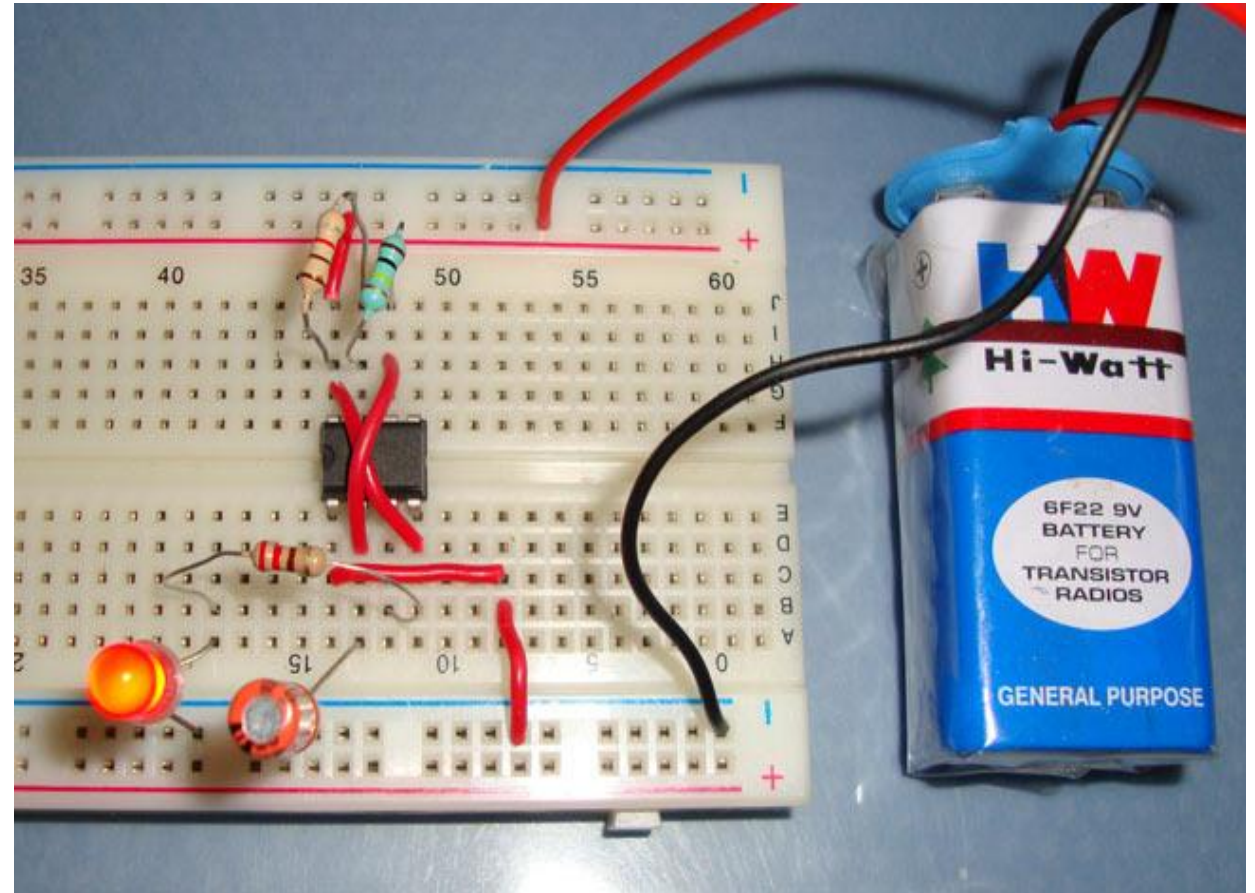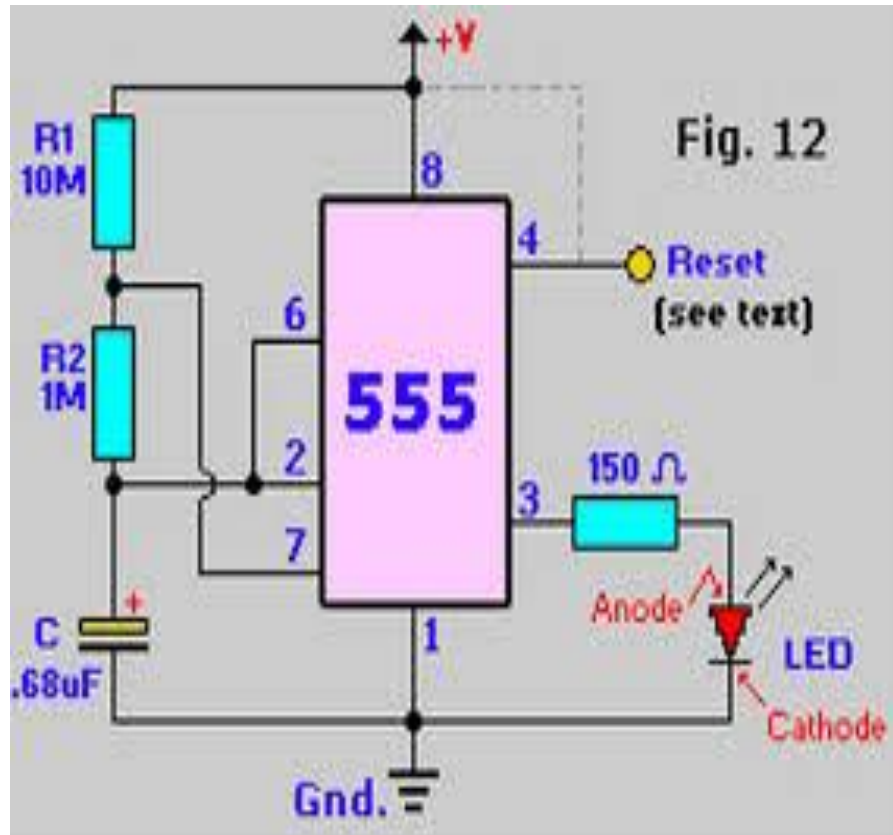

Design a astable for frequency of 5 KHz and 75% duty cycle.

frequency = 5KHz  
$$\frac{1}{T} = \frac{1}{5KHz} = 0.2 \text{ ms}$$

$$0.2 \text{ ms} = T_{on} + T_{off}$$

$$T_{on} = 75\% \times 0.2 \text{ ms}$$
$$= 0.75 \times 0.2$$
$$= 0.15 \text{ ms}$$


$$T_{off} = 0.25 \times 0.2$$
$$= 0.05 \text{ ms}$$

but  $t_{off} = 0.693 \times R_b \times C$   
assume  $C = 0.1 \mu\text{F}$

$$0.05 = 0.693 \times R_b \times 0.1 \times 10^{-6}$$

$$\frac{0.05 \times 10^{-3}}{0.693 \times 0.1 \times 10^{-6}} = R_b$$

$$721.5 \text{ } \Omega = R_b$$

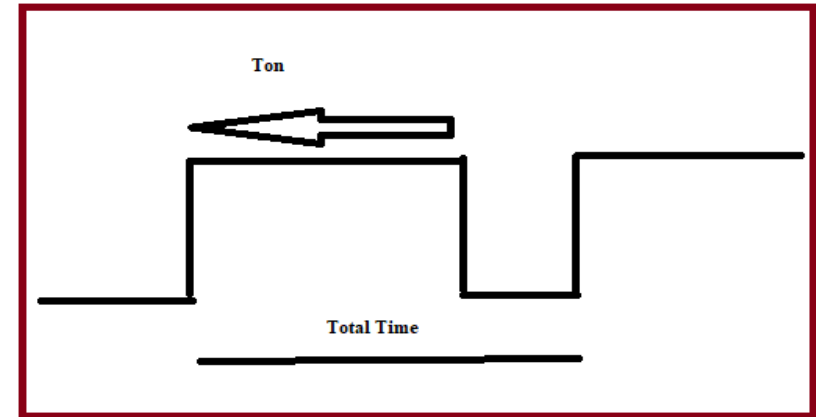


$$721.5 \Omega = R_b.$$

$$T_{on} = 0.693 (R_a + R_b) C$$

$$0.15 \times 10^{-3} = 0.693 (R_a + 721.5) 0.1 \times 10^{-6}.$$

$$R_a = 1.443 \text{ k}\Omega.$$

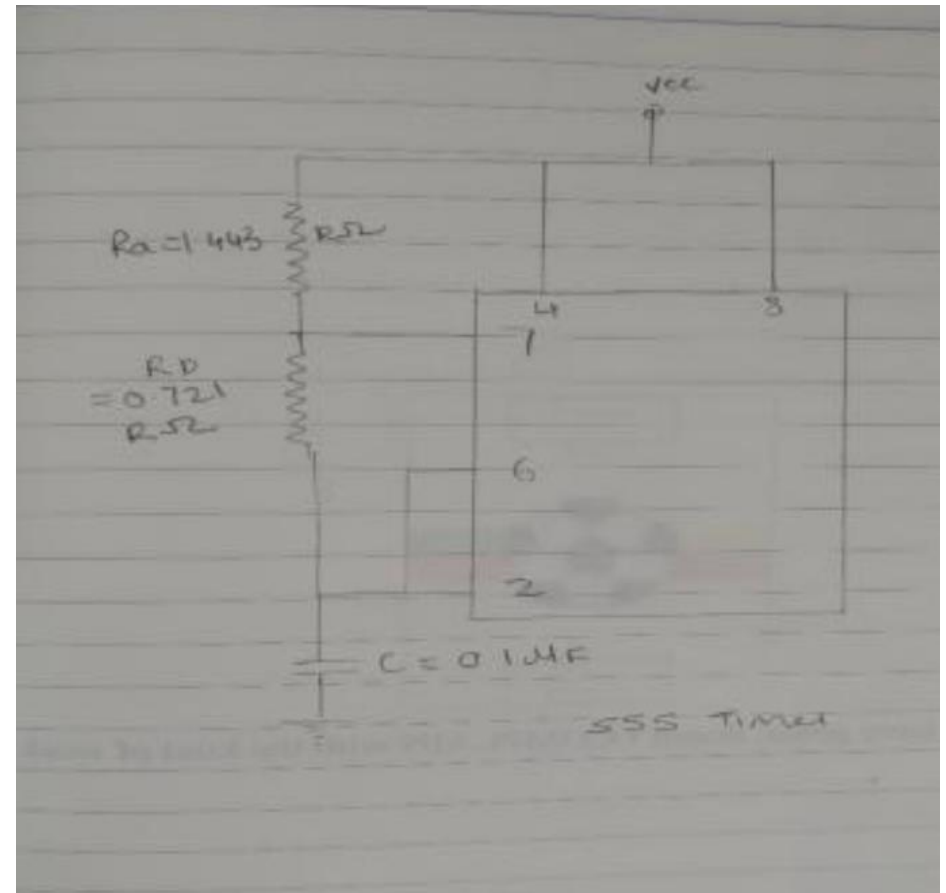

---

THANK YOU

