

# Working of 555 Timer

(Unit IV)

Prof Suneeta S. Raykar,  
Associate Professor E&E GEC  
Suneeta@gec.ac.in

# Contents

- Need to study 555.
- Pin diagram.
- Block diagram.
- Working of 555 timer

# Introduction to IC 555

- The 555 timer IC was introduced in the year 1970 by Signetic Corporation and gave the name **SE/NE 555 timer**.
- It is basically a monolithic timing circuit that produces accurate and highly stable time delays or oscillation.
- When compared to the applications of an op-amp in the same areas, the 555 IC is also equally reliable and is cheap in cost. And works with single power supply (+Vcc only)
- Apart from its applications as a **monostable multivibrator** and **astable multivibrator**, a 555 timer can also be used in **dc-dc converters**, **digital logic probes**, **waveform generators**, analog frequency meters and tachometers, **temperature measurement** and control devices, **voltage regulators** etc.

**Able to generate precise time duration of HIGH and LOW output, from micro seconds to hours, that's why 555 is very popular and versatile IC.**

# IC 555 details

- The timer IC is set up to work in either of the two modes
  - – one-shot or monostable or as a free-running or astable multivibrator.
- The **SE 555** can be used for temperature ranges between  $-55^{\circ}\text{C}$  to  $125^{\circ}$ .
- The **NE 555** can be used for a temperature range between  $0^{\circ}$  to  $70^{\circ}\text{C}$ .




# Features of 555

- Power supply ranging from + 5 Volts to + 18 Volts supply voltage.
- Sinking or sourcing 200 mA of load current.
- The external components should be selected properly so that the timing intervals can be made into several minutes along with the frequencies exceeding several hundred kilohertz.
- The output of a 555 timer can drive a transistor-transistor logic (TTL) due to its high current output.
- It has a temperature stability of 50 parts per million (ppm) per degree Celsius change in temperature, or equivalently 0.005 %/ °C.
- The duty cycle of the timer is adjustable.
- The maximum power dissipation per package is 600 mW and its trigger and reset inputs has logic compatibility. More features are listed in the datasheet.
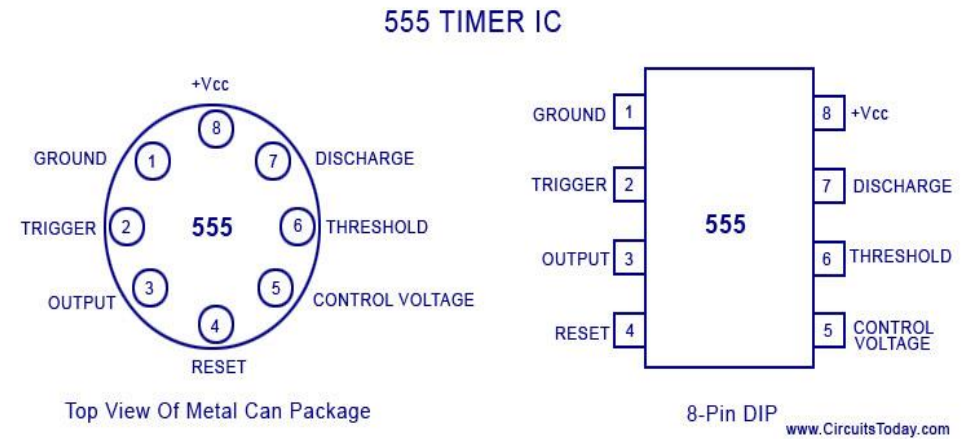
# 555 pin details

The 555 Timer IC is available as an 8-pin metal can, an 8-pin mini DIP (dual-in-package).



- **Pin 1, ground terminal**
- **Pin 2: Trigger Terminal:** The trigger pin is used to feed the trigger input when the 555 IC is set up as a monostable multivibrator.
- **Pin 3: Output Terminal:** Output of the timer is available at this pin. There are two ways in which a load can be connected to the output terminal.
- **Pin 4: Reset Terminal:** Whenever the timer IC is to be reset or disabled, a negative pulse is applied to pin 4, and thus is named as reset terminal. When this pin is not to be used for reset purpose, it should be connected to  $+V_{CC}$  to avoid any possibility of false triggering.
- **Pin 5: Control Voltage Terminal:** The threshold and trigger levels are controlled using this pin. The pulse width of the output waveform is determined by connecting a POT or bringing in an external voltage to this pin.


# 555- Pin details.

- **Pin 6: Threshold Terminal:** This is the non-inverting input terminal of comparator 1, which compares the voltage applied to the terminal with a reference voltage of  $\frac{2}{3} V_{CC}$ . The amplitude of voltage applied to this terminal is responsible for the set state of flip-flop.
- **Pin 7 : Discharge Terminal:** This pin is connected internally to the collector of transistor and mostly a capacitor is connected between this terminal and ground. It is called discharge terminal because when transistor saturates, capacitor discharges through the transistor.
- **Pin 8: Supply Terminal:** A supply voltage of + 5 V to + 18 V is applied to this terminal with respect to ground (pin 1).





# SR flip flop working

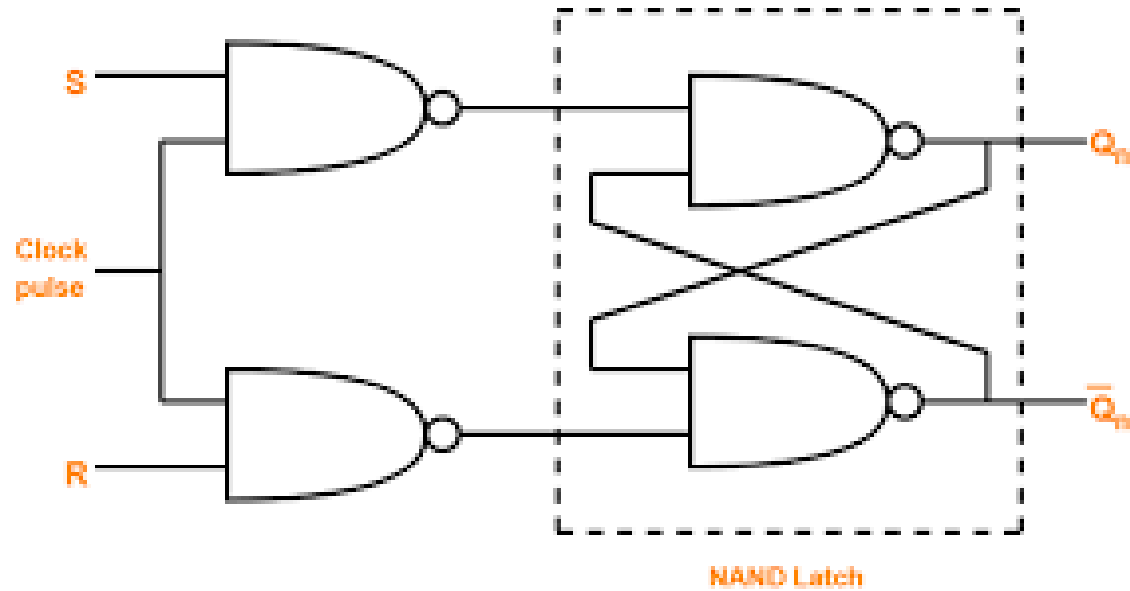

SR Flip Flop Using NAND Latch

S	R	Q	Q'
1	0	1	0
0	0	1	0
0	1	0	1
0	0	0	1
1	1	0	0


After S = 1 and R = 0

After S = 0 and R = 1

Invalid

# Working of 555 timer

555 IC Timer Block Diagram

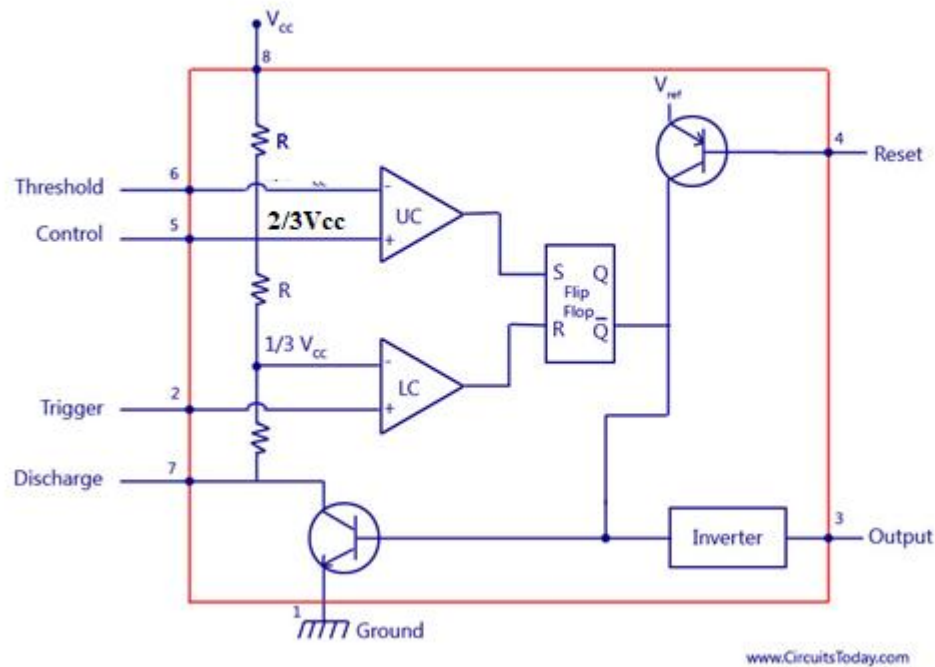

Upper comparator has a threshold input (pin 6) and a control input (pin 5).

Output of the upper comparator is applied to set (S) input of the flip-flop.

Whenever the threshold voltage exceeds the control voltage, the upper comparator will set the flip-flop and its output is high.

$Q'$  from the flip-flop when given to the base of the discharge transistor saturates it and thus discharges the transistor that is connected externally to the discharge pin 7.

- The complementary signal out of the flip-flop goes to pin 3, the output. The output available at pin 3 is low. These conditions will prevail until lower comparator triggers the flip-flop. Even if the voltage at the threshold input falls below  $(2/3) V_{CC}$ , that is upper comparator cannot cause the flip-flop to change again. It means that the upper comparator can only force the flip-flop's output high.

Output of both the comparators is supplied to the flip-flop.

Flip-flop assumes its state according to the output of the two comparators.

One of the two transistors is a discharge transistor of which collector is connected to **pin 7**.

This transistor saturates or cuts-off according to the output state of the flip-flop.

The saturated transistor provides a discharge path to a capacitor connected externally. Base of another transistor is connected to a reset terminal.

A pulse applied to this terminal resets the whole timer irrespective of any input.

THANK YOU